

## Boolean Algebra

### Exercises :

1. Determine the values of  $A, B, C$  &  $D$  that make the sum term  $A + \bar{B} + C + \bar{D}$  equal to 0 ?

Soln;  $A + \bar{B} + C + \bar{D} = 0$   
 $\Rightarrow \begin{matrix} \downarrow & \downarrow & \downarrow & \downarrow \\ 0 & 0 & 0 & 0 \end{matrix}$  so  $\begin{matrix} A=0 & C=0 \\ B=1 & D=1 \end{matrix}$

what about  $A \bar{B} C \bar{D} = 1$   
 $\begin{matrix} \downarrow & \downarrow & \downarrow & \downarrow \\ 1 & 1 & 1 & 1 \end{matrix}$  so  $\begin{matrix} A=1 & C=1 \\ B=0 & D=0 \end{matrix}$

2. Apply DeMorgan's Theorem to each of the following expressions:

-  $\overline{(A+B+C)D} = \bar{A} \bar{B} \bar{C} + \bar{D}$

-  $\overline{A\bar{B} + \bar{C}D + \bar{E}F} = \overline{A\bar{B}} \cdot \overline{(\bar{C}D)} \cdot \overline{\bar{E}F}$   
 $= (\bar{A} + B) (C + \bar{D}) (\bar{\bar{E}} + \bar{\bar{F}})$


-  $\overline{(A+B) \bar{C} \bar{D} + \bar{E} + \bar{F}} = \overline{(A+B)} \cdot \overline{\bar{C} \bar{D}} \cdot \bar{\bar{E}} \cdot \bar{\bar{F}}$   
 $= ((\bar{A} + \bar{B}) + C + D) \cdot \bar{\bar{E}} \cdot \bar{\bar{F}}$   
 $= (\bar{A} \bar{B} + C + D) \bar{\bar{E}} \cdot \bar{\bar{F}}$

3. Use DeMorgan's Law & other Boolean laws to develop an expression for the exclusive-NOR gate.

soln: exclusive OR gate: XOR :  $A \oplus B = A\bar{B} + \bar{A}B$

$$\begin{aligned} \text{NOR gate: } \overline{A\bar{B} + \bar{A}B} &= \overline{A\bar{B}} \cdot \overline{\bar{A}B} \\ &= (\bar{A} + B)(A + \bar{B}) \\ &= \underbrace{\bar{A}A}_{0} + \bar{A}\bar{B} + B\bar{A} + \underbrace{B\bar{B}}_{0} \\ &= \bar{A}\bar{B} + AB \end{aligned}$$

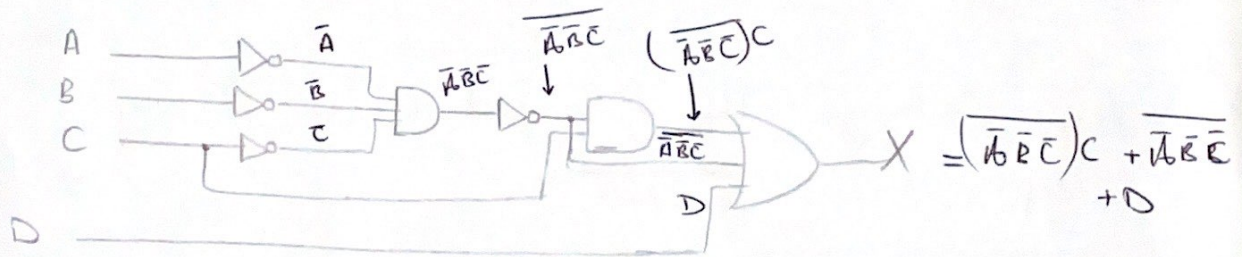
4. Reduce the following logic circuit to a minimum form.



Simply X to a minimum form:

$$\begin{aligned} X &= (\bar{A}\bar{B}\bar{C})C + \bar{A}\bar{B}\bar{C} + D \\ &= (\bar{A} + \bar{B} + \bar{C})C + (\bar{A} + \bar{B} + \bar{C}) + D \\ &= (\bar{A} + \bar{B} + \bar{C})(\underbrace{C + 1}_1) + D \\ &= A + B + C + D \end{aligned}$$

Equivalent to

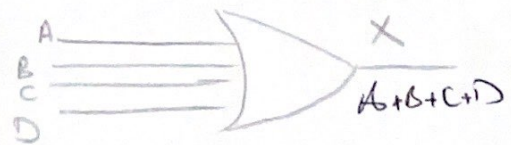







⑤ Use NAND gates to implement each expression: (you can use negation gate).


(i)  $X = \bar{A} + B$

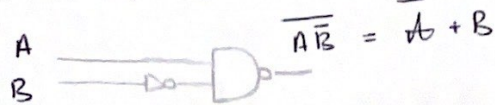

(ii)  $X = \bar{A}B$

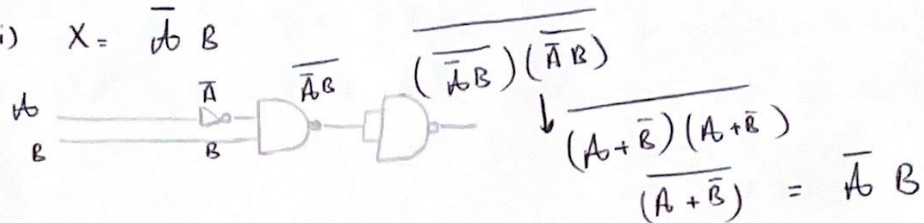

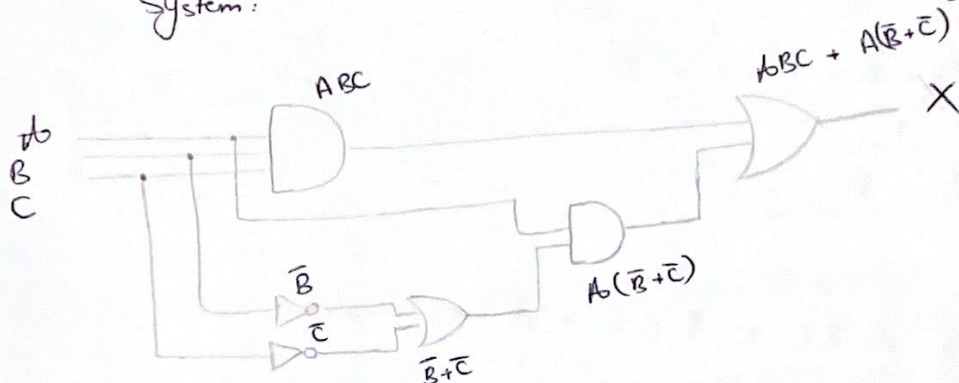⑥ Find the Boolean algebra expression for the following system:



Simplify & construct the truth table for this logic circuit.

$ABC + A(\bar{B} + \bar{C})$   
 $ABC + A(\overline{BC})$   
 $A(\underbrace{BC + \overline{BC}}_1)$   
 $A \cdot 1$   
 $= \underline{\underline{A}}$



⑦ Simplify : ①  $(A\bar{B}(C+BD) + \bar{A}\bar{B})C$

Soln:  $(A\bar{B}C + \underbrace{A\bar{B}BD}_{0} + \bar{A}\bar{B})C$

$$\begin{aligned}(A\bar{B}C + \bar{A}\bar{B})C &= A\bar{B}\underline{CC} + \bar{A}\bar{B}C \\&= A\bar{B}C + \bar{A}\bar{B}C \\&= \underbrace{(A + \bar{A})}_{1}\bar{B}C = \bar{B}C\end{aligned}$$

②  $\overline{AB + AC} + \bar{A}\bar{B}C$

$$(\bar{A} + \bar{B})(\bar{A} + \bar{C}) + \bar{A}\bar{B}C$$

$$\bar{A}\bar{A} + \bar{A}\bar{C} + \bar{B}\bar{A} + \bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$\bar{A} + \bar{A}\bar{C} + \bar{B}\bar{A} + \bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$\bar{A}(1 + \bar{C} + \bar{B} + \bar{A}\bar{B}) + \bar{B}\bar{C}$$

$$\boxed{\bar{A} + \bar{B}\bar{C}}$$

③  $\bar{A}BC + \underbrace{A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + A\bar{B}C}_{(A+\bar{A})\bar{B}\bar{C}}$

$$\left| \begin{array}{c} \underbrace{(A+\bar{A})}_{1}\bar{B}\bar{C} \\ \bar{B}\bar{C} \\ \hline \underbrace{(\bar{A}+A)}_{1}BC \end{array} \right|$$

$\therefore \bar{B}\bar{C} + BC + \underbrace{A\bar{B}C}_{\bar{B}\bar{C}}$

$$\bar{B}(\bar{C} + AC) + BC$$

$$\downarrow \text{law}$$

$$\bar{B}(\bar{C} + A) + BC$$

$$\bar{B}\bar{C} + \bar{B}A + BC$$



Recall: ① The Sum of Product Form SOP

examples:  $AB + ABC \rightarrow \text{domain } A, B, C$

$ABC + CD\bar{E} \rightarrow \text{domain } A, B, C, D, \bar{E}$


$\bar{B}C\bar{D} + AB + DC \rightarrow \text{domain } A, B, C, D$

Note that SOP can contain


single complement  $\bar{A}$  not  $\overline{AB}$

\* AND/OR implementation of an SOP expression:

$$X = AB + BCD + AC$$

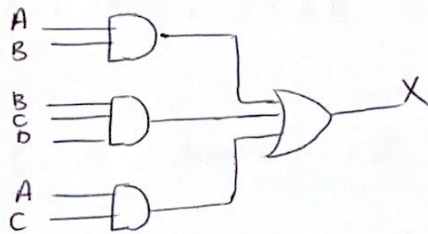

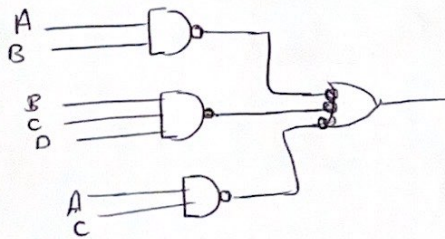\* NAND/NOR implementation of  $X = AB + BCD + AC$



Def: A standard SOP expression is one in which all the variables in the domain appear in each product term in the expression.

e.g:  $\bar{A}BC\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$

\* Convert the following to standard SOP:

$$\underbrace{A \bar{B} C}_{D \text{ is missing}} + \underbrace{\bar{A} \bar{B}}_{C \& D \text{ are missing}} + A \bar{B} C D$$

Soln: we use trick  $(C + \bar{C} = 1)$

$$A \bar{B} C (D + \bar{D}) = A \bar{B} C D + A \bar{B} C \bar{D}$$

$$\begin{aligned} \bar{A} \bar{B} (C + \bar{C}) &= [\underbrace{\bar{A} \bar{B} C + \bar{A} \bar{B} \bar{C}}_{\bar{A} \bar{B} C D + \bar{A} \bar{B} C \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} \bar{B} \bar{C} \bar{D}}] (D + \bar{D}) \\ &= \bar{A} \bar{B} C D + \bar{A} \bar{B} C \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} \bar{B} \bar{C} \bar{D} \end{aligned}$$

Hence,  $\rightarrow A \bar{B} C D + A \bar{B} C \bar{D} + \bar{A} \bar{B} C D + \bar{A} \bar{B} C \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} \bar{B} \bar{C} \bar{D}$

\* Binary Representation of a SOP (standard form)

$\rightarrow$  Determine the binary values for which the following SOP expression is equal to 1.

$$A C B D + A \bar{B} \bar{C} D + \bar{A} \bar{B} \bar{C} \bar{D} = 1$$

$\underbrace{A C B D}_{=1}$	$\underbrace{A \bar{B} \bar{C} D}_{=1}$	$\underbrace{\bar{A} \bar{B} \bar{C} \bar{D}}_{=1}$
$\therefore A=1$	$A=1$	$A=0$
$B=1$	$B=0$	$B=0$
$C=1$	$C=0$	$C=0$
$D=1$	$D=1$	$D=0$

SOP equal 1 when any or all of the three product terms is 1.




## 2] The Product of Sums (POS)

examples:  $(\bar{A} + B)(A + \bar{B} + C) \rightsquigarrow \text{domain } A, B, C$

$(\bar{A} + \bar{B} + \bar{C})(C + \bar{D} + E)(\bar{B} + C + D) \rightsquigarrow \text{domain } A, B, C, D, E$

$$X = (A + B)(B + C + D)(A + C)$$

AND implementation:

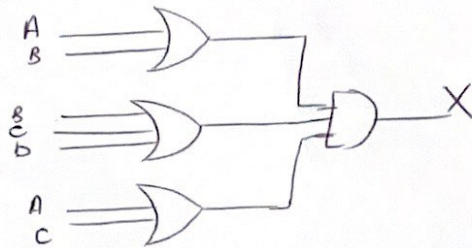

The Standard POS Form:

Def: A standard POS expression is one in which all the variables in the domain appear in each term in the expression.

\* Convert to the standard POS form:

$$\underbrace{(A + \bar{B} + C)}_{+ D\bar{D}} \underbrace{(\bar{B} + C + \bar{D})}_{+ A\bar{A}} \underbrace{(A + \bar{B} + \bar{C} + D)}_{\checkmark}$$

$$(A + \bar{B} + C + D\bar{D})(\bar{B} + C + \bar{D} + A\bar{A})$$

$$(A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(\bar{B} + C + \bar{D} + A)(\bar{B} + C + \bar{D} + \bar{A})(A + \bar{B} + \bar{C} + D)$$

\* Binary representation for POS :-

Determine the binary values of the variables for which the following standard POS expression is equal to 0:

$$\underbrace{(A+B+C+D)}_0 \quad \underbrace{(A+\bar{B}+\bar{C}+D)}_0 \quad \underbrace{(\bar{A}+\bar{B}+\bar{C}+\bar{D})}_0$$

↓		
A=0	A=0	A=1
B=0	B=1	B=1
C=0	C=1	C=1
D=0	D=0	D=1

The POS expression equals 0 when any of the three terms equals 0.